Intro Microelectronic Circuits with Laboratory

A Simple MOS Differential Amplifier

Elias Tuthill[1] **and Henry Tejada Deras**[1]

[1]*Franklin W. Olin College of Engineering*

1. Voltage Transfer Characteristics

1.1. Results

1.2. Analysis

1.3. Discussion

2. Transconductance, Output Resistance, and Gain

2.1. Results

2.2. Analysis

2.3. Discussion

3. Unity-Gain Follower

3.1. Results

3.2. Analysis

3.3. Discussion