Intro Microelectronic Circuits with Laboratory

A Current-Mirror Differential Amplifier

Henry Tejada Deras[1] **and Elias Tuthill**[1]

[1]*Franklin W. Olin College of Engineering*

1. Voltage Transfer Characteristics

1.1. Results

1.2. Analysis

1.3. Discussion

2. Transconductance, Output Resistance, and Gain

2.1. Results

2.2. Analysis

2.3. Discussion

3. Unity-Gain Follower Step Response

3.1. Results

3.2. Analysis

3.3. Discussion